

**Question:**

Science Class 6

Bulb glows only in

- 1 closed circuit
- 2 open circuit
- 3 in both circuits
- 4 open circuit if bulb is not fused

*Downloaded From: eLearn Pro ( <https://myelearnpro.com/> )*

**eLearn Pro**  
Learning Made Easy

*\* Some Hindi Fonts are not rendered properly.*

*Downloaded From: eLearn Pro ( <https://myelearnpro.com/> )*