

Question:**Physics**

Which of the following circuit elements is used to 'block DC in an electronic circuit?

- 1 Resistances
- 2 Capacitance
- 3 Inductance
- 4 Diode

Downloaded From: eLearn Pro (<https://myelearnpro.com/>)

eLearn Pro
Learning Made Easy

** Some Hindi Fonts are not rendered properly.*

Downloaded From: eLearn Pro (<https://myelearnpro.com/>)